


Module #12 : Verilog HDL Component Inference

12.1: Latches:

- A latch is inferred (put into the synthesized circuit) if a variable, or one of its bits, is not assigned in all branch of an if statement.
- A latch is also inferred in a case statement if a variable is assigned to in only some of the branches.
- To improve code readability, use the if statement to synthesize a latch because it is difficult to explicitly specify the latch enable signal using a case statement

 Example 12 .1:


```
always @(clk,d)
begin
    if (clk)
        q <= d;
end
```



Module #12 : Verilog HDL Component Inference

 Example 12 .2:

```
always @(clk or rst or d)  
begin  
  if (rst)  
    q <= 0;  
  else if (clk)  
    q <= d;  
end
```




Module #12 : Verilog HDL Component Inference

12.2: Edge-Triggered Registers, Flip-flops, Counters:

- A register (flip-flop) is inferred by using posedge or negedge clause for the clock in the event list of an always block. To add an asynchronous reset, include a second posedge/negedge for the reset and use the if (reset) ... else statement.
- Note that when you use the negedge for the reset (active low reset), the if condition is (!reset).

 Example 12.3:


```
always @(posedge clk)
begin;
  a <= b & c;
end
```



Module #12 : Verilog HDL Component Inference

 Example 12.4:

```
always @(posedge clk or negedge rst);  
begin;  
    if (! rst)  
        a <= 0;  
    else  
        a <= b & c;  
end
```



Module #12 : Verilog HDL Component Inference

Example 12 .5:

```
reg [7:0] count;  
wire enable;  
always @(posedge clk or posedge rst) // Do not include enable.  
begin;  
    if (rst)  
        count <= 0;  
    else if (enable)  
        count <= count+1;  
end; // 8 flip-flops will be generated
```

Module #12 : Verilog HDL Component Inference


12.3: Multiplexers:

- A multiplexer is inferred by assigning a variable to different variables/values in each branch of an if or case statement.
- You can avoid specifying each and every possible branch by using the else and default branches.
- To improve readability of your code, use the case statement to model large multiplexers

Note that a latch will be inferred if a variable is not assigned to for all the possible branch conditions.

 Example 12 .6:


```
if (sel == 1)
    y = a;
else
    y = b;
```



Module #12 : Verilog HDL Component Inference

 Example 12 .7:

```
case (sel)
  2'b00: y = a;
  2'b01: y = b;
  2'b10: y = c;
  default: y = d;
endcase
```



Module #12 : Verilog HDL Component Inference

12.4: Adders/Subtractors:

- The $+$ / $-$ operators infer an adder/subtractor whose width depend on the width of the larger operand


Example 12.8:

if (*sel* == 1)

y = *a* + *b*;

else


y = *c* + *d*;

 

Module #12 : Verilog HDL Component Inference

 Example 12.9:

```
if (sel == 1)
    y = a + b;
else
    y = c + d;
```



Module #12 : Verilog HDL Component Inference

12.5: Tri-State Buffers:

- A tristate buffer is inferred if a variable is conditionally assigned a value of z using an if, case or conditional operator.

Example 12 .10:

```
if(en == 1)
    y = a;
else
    y = 1'bz;
```

