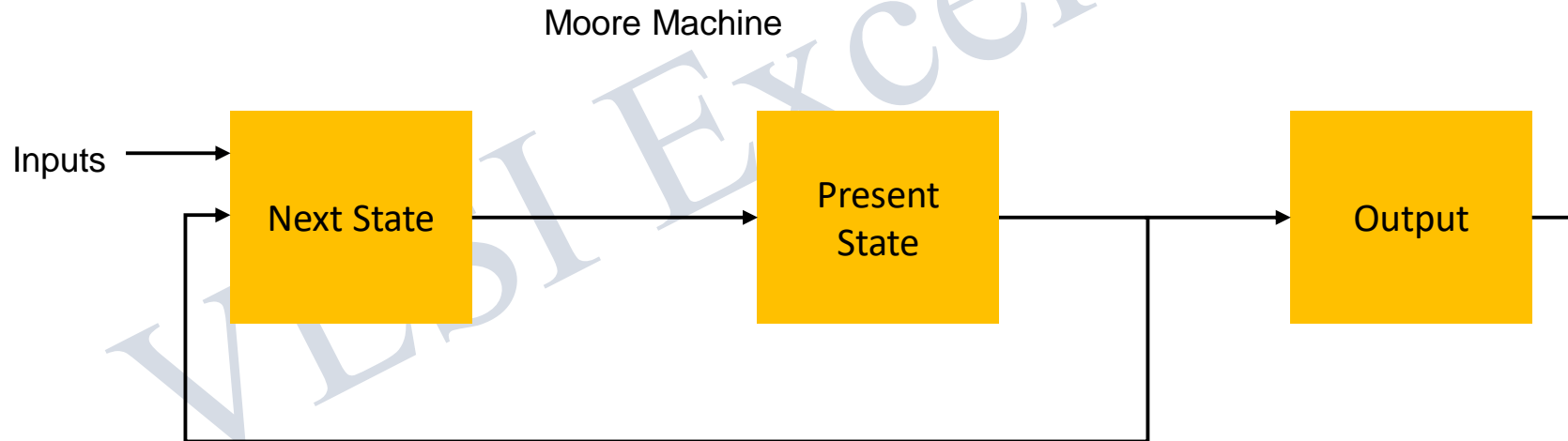


Module #13 : Verilog HDL 1001 Sequence Detector

13.1: Moore FSM:


- In Moore FSM, output depends only on the present state
- Output is less prone to glitch because of registered present state
- More number of states are required
- They react slower to inputs (One clock cycle later)



Module #13 : Verilog HDL 1001 Sequence Detector

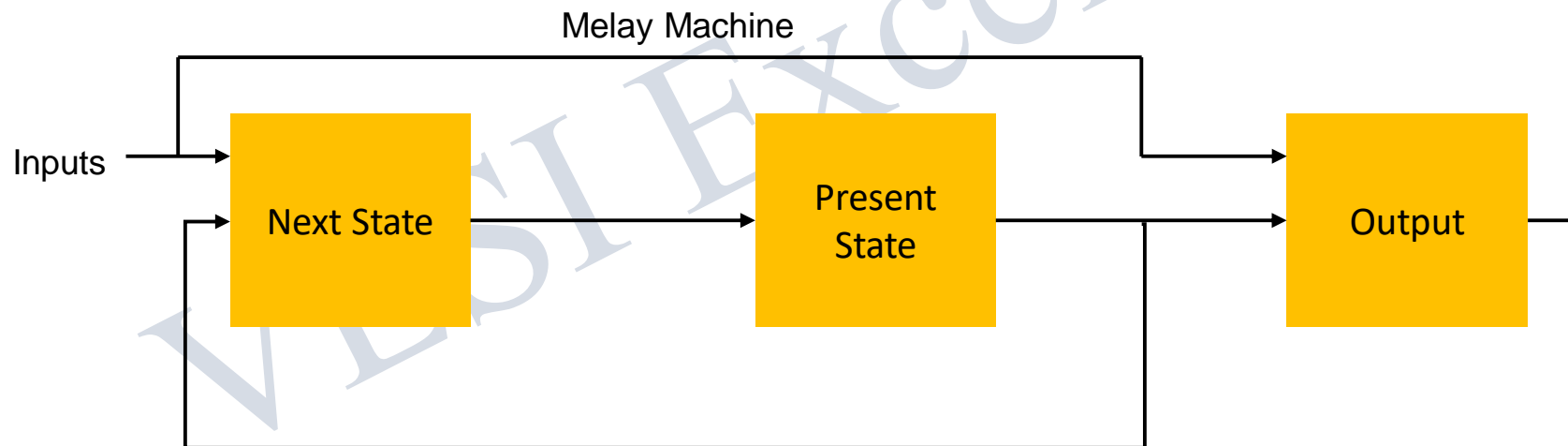13.2: Mealy FSM:

- In Mealy FSM, output depends on the present state as well as present input
- Output is more prone to glitch because of asynchronous dependency on present input
- Less number of states are required
- They react faster to inputs



Module #13 : Verilog HDL 1001 Sequence Detector


13.3: Verilog FSM Design Techniques :

- 1) Using a Single Process (Procedural Block) to Code Present State, Next State and Output Logic
- 2) Using Two Process, One to code Present State and Next State logic and another to code Output Logic,
- 3) Using Three Process each to code Present State, Next State and Output Logic

Note: When modeling finite state machines, it is recommended to separate the sequential current-state logic from the combinational next-state and output logic.

Module #13 : Verilog HDL 1001 Sequence Detector

 13.4: 1001 Sequence Detector *Moore (Non-Overlapping)* FSM Diagram :



S0 – On Reset

S1 – 1 is detected

S2 – 10 is detected

S3 – 100 is detected

S4 – 1001 is detected

Module #13 : Verilog HDL 1001 Sequence Detector

13.5: 1001 Sequence Detector Moore (Non Overlapping) Verilog Code :

Example 13.1:

```
module moore_1001_nonovr (clk, rst, data_i, data_o);  
input clk, rst, data_i;  
output data_o; // data_o is declared reg so that it can  
reg data_o; // be assigned in an always block.  
parameter S0=0, S1=1, S2=2, S3=3, S4 = 4;  
reg [2:0] state, nxt_st;  
always @ (state or data_i)  
begin : next_state_logic //Name of always procedure.  
case (state)  
S0: begin  
if (data_i) nxt_st = S1;  
else nxt_st = S0;  
end
```

```
S1: begin  
if(data_i) nxt_st = S1;  
else nxt_st = S2;  
end  
S2: begin  
if (data_i) nxt_st = S1;  
else nxt_st = S3;  
end  
S3: begin  
if (data_i) nxt_st = S3;  
else nxt_st = S0;  
end  
S4: begin  
if (data_i) nxt_st = S1;  
else nxt_st = S0;  
end  
default: nxt_st = S0;  
endcase  
end  
// default is optional since  
//all 4 cases are covered  
//specifically. Good practice  
// says uses it
```

Module #13 : Verilog HDL Finite State Machines (FSMs)


13.5: 1001 Sequence Detector Moore (Non Overlapping) Verilog Code :

```
always @(posedge clk or posedge rst)  
begin : register_generation  
if (rst) state = S0;  
else state = nxt_st;  
end
```

```
always @(state) begin : output_logic  
case (state)  
S0: data_o = 1'b0;  
S1: data_o = 1'b0;  
S2: data_o = 1'b0;  
S3: data_o = 1'b0;  
S4: data_o = 1'b1;  
default: data_o = 1'b0;; // default avoids latches  
endcase  
end  
endmodule
```

Module #13 : Verilog HDL 1001 Sequence Detector

 13.4: 1001 Sequence Detector *Moore (Overlapping)* FSM Diagram :



S0 – On Reset

S1 – 1 is detected

S2 – 10 is detected

S3 – 100 is detected

S4 – 1001 is detected

Module #13 : Verilog HDL 1001 Sequence Detector

13.5: 1001 Sequence Detector Moore (Overlapping) Verilog Code :

Example 13.2:

```
module moore_1001_ovr (clk, rst, data_i, data_o);  
input clk, rst, data_i;  
output data_o; // data_o is declared reg so that it can  
reg data_o; // be assigned in an always block.  
parameter S0=0, S1=1, S2=2, S3=3, S4 = 4;  
reg [2:0] state, nxt_st;  
always @ (state or data_i)  
begin : next_state_logic //Name of always procedure.  
case (state)  
S0: begin  
if (data_i) nxt_st = S1;  
else nxt_st = S0;  
end
```

```
S1: begin  
if(data_i) nxt_st = S1;  
else nxt_st = S2;  
end  
S2: begin  
if (data_i) nxt_st = S1;  
else nxt_st = S3;  
end  
S3: begin  
if (data_i) nxt_st = S3;  
else nxt_st = S0;  
end  
S4: begin  
if (data_i) nxt_st = S1;  
else nxt_st = S2;  
end  
default: nxt_st = S0;  
endcase  
end  
// default is optional since  
//all 4 cases are covered  
//specifically. Good practice  
// says uses it
```


Module #13 : Verilog HDL Finite State Machines (FSMs)


13.5: 1001 Sequence Detector Moore (Overlapping) Verilog Code :

```
always @(posedge clk or posedge rst)  
begin : register_generation  
if (rst) state = S0;  
else state = nxt_st;  
end
```

```
always @(state) begin : output_logic  
case (state)  
S0: data_o = 1'b0;  
S1: data_o = 1'b0;  
S2: data_o = 1'b0;  
S3: data_o = 1'b0;  
S4: data_o = 1'b1;  
default: data_o = 1'b0;; // default avoids latches  
endcase  
end  
endmodule
```

Module #13 : Verilog HDL 1001 Sequence Detector

 13.4: 1001 Sequence Detector *Mealy* (Non-Overlapping) FSM Diagram :



S0 – On Reset

S1 – 1 is detected

S2 – 10 is detected

S3 – 100 is detected

Module #13 : Verilog HDL 1001 Sequence Detector

13.5: 1001 Sequence Detector Mealy (Non Overlapping) Verilog Code :

Example 13.3:

```
module mealy_1001_nonovr (clk, rst, data_i, data_o);  
input clk, rst, data_i;  
output data_o; // data_o is declared reg so that it can  
reg data_o; // be assigned in an always block.  
parameter S0=0, S1=1, S2=2, S3=3, S4 = 4;  
reg [2:0] state, nxt_st;  
always @ (state or data_i)  
begin : next_state_logic //Name of always procedure.  
case (state)  
S0: begin  
if (data_i) nxt_st = S1;  
else nxt_st = S0;  
end
```

```
S1: begin  
if(data_i) nxt_st = S1;  
else nxt_st = S2  
end  
S2: begin  
if (data_i) nxt_st = S1;  
else nxt_st = S3;  
end  
S3: begin  
if (data_i) nxt_st = S0;  
else nxt_st = S0;  
end  
default: nxt_st = S0;  
endcase  
end  
// default is optional since  
//all 4 cases are covered  
//specifically. Good practice  
// says uses it
```

Module #13 : Verilog HDL Finite State Machines (FSMs)


13.5: 1001 Sequence Detector Mealy (Non Overlapping) Verilog Code :

```
always @(posedge clk or posedge rst)  
begin : register_generation  
if (rst) state = S0;  
else state = nxt_st;  
end
```

```
always @(state or data_i) begin : output_logic  
case (state)  
S0: data_o = 1'b0;  
S1: data_o = 1'b0;  
S2: data_o = 1'b0;  
S3: begin  
    if(data_i) data_o = 1'b1;  
    else data_o = 1'b0;  
end  
default: data_o = 1'b0;; // default avoids latches  
endcase  
end  
endmodule
```

Module #13 : Verilog HDL 1001 Sequence Detector

 13.4: 1001 Sequence Detector *Mealy (Overlapping)* FSM Diagram :



S0 – On Reset

S1 – 1 is detected

S2 – 10 is detected

S3 – 100 is detected

Module #13 : Verilog HDL 1001 Sequence Detector

13.5: 1001 Sequence Detector Mealy (Overlapping) Verilog Code :

Example 13.4:

```
module mealy_1001_ovr (clk, rst, data_i, data_o);  
input clk, rst, data_i;  
output data_o; // data_o is declared reg so that it can  
reg data_o; // be assigned in an always block.  
parameter S0=0, S1=1, S2=2, S3=3, S4 = 4;  
reg [2:0] state, nxt_st;  
always @ (state or data_i)  
begin : next_state_logic //Name of always procedure.  
case (state)  
S0: begin  
if (data_i) nxt_st = S1;  
else nxt_st = S0;  
end
```

```
S1: begin  
if(data_i) nxt_st = S1;  
else nxt_st = S2;  
end  
S2: begin  
if (data_i) nxt_st = S1;  
else nxt_st = S3;  
end  
S3: begin  
if (data_i) nxt_st = S1;  
else nxt_st = S0;  
end  
default: nxt_st = S0;  
endcase  
end  
// default is optional since  
//all 4 cases are covered  
//specifically. Good practice  
// says uses it
```

Module #13 : Verilog HDL Finite State Machines (FSMs)

13.5: 1001 Sequence Detector Mealy (Non Overlapping) Verilog Code :

```
always @(posedge clk or posedge rst)  
begin : register_generation  
if (rst) state = S0;  
else state = nxt_st;  
end
```

```
always @(state or data_i) begin : output_logic  
case (state)  
S0: data_o = 1'b0;  
S1: data_o = 1'b0;  
S2: data_o = 1'b0;  
S3: begin  
    if(data_i) data_o = 1'b1;  
    else data_o = 1'b0;  
end  
default: data_o = 1'b0;; // default avoids latches  
endcase  
end  
endmodule
```